

Chapter 6: **Digital Arithmetic: Operations & Circuits**

Prof. Dr. Aloke Kumar Saha

Professor

Department of CSE

University of Asia Pacific (UAP)

Chapter 6 Objectives

- *Selected areas covered in this chapter:*
 - Binary addition, subtraction, multiplication, division.
 - Differences between binary addition and OR addition.
 - Basic operation of a half adder circuit.
 - Basic operation of a full adder circuit.
 - Operation of a parallel adder circuit.
 - Operation of a parallel subtractor circuit.
 - Operation of a parallel adder/subtractor circuit.
 - Operation of a BCD adder circuit.
 - ALU integrated circuits for various logic and arithmetic operations on input data.

6-1 Binary Addition

- Binary numbers are added like decimal numbers.
 - In decimal, when numbers sum more than 9, a carry results.
 - In binary when numbers sum more than 1, a carry takes place.
- Addition is the basic arithmetic operation used by digital devices for subtraction, multiplication & division.

6-1 Binary Addition

Four possible situations when addition one bit to another in any position of a binary number.

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

For uniformity

$$0 + 0 = 00$$

$$0 + 1 = 01$$

$$1 + 0 = 01$$

$$1 + 1 = 10$$


6-2 Design of a Half Adder

- Construct a truth table...
 - 2 inputs (2 numbers to be added).
 - 2 outputs (sum and carry).

Augend Bit Input A	Added Bit Input B		Sum Bit Output S	Carry Bit Output C
0	0		0	0
0	1		1	0
1	0		1	0
1	1		0	1

 6-2 Design of a Half Adder

- $S = A'B + AB' = A \oplus B$
- $C = AB$
- Now Draw the Circuit.



6-3 Design of a Full Adder

- Construct a truth table...
 - 3 inputs (2 numbers to be added and carry in).
 - 2 outputs (sum and carry out).

Augend bit input	Addend bit input	Carry bit input		Sum bit output	Carry bit output
A	B	C _{IN}		S	C _{OUT}
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1

6-3 Design of a Full Adder

- Use algebraic methods or K-maps to simplify the resulting SOP form.
 - The result is the logic circuit shown here.

K-map for Cout:

	$A'B'$	AB'	AB	$A'B$
$C'in$	0	0	1	0
Cin	0	1	1	1

There are 3 pairs. So the result is
 $Cout = AB + ACin + BCin$



6-3 Design of a Full Adder

- K-map for Sum:

	$A'B'$	AB'	AB	$A'B$
$C'in$		1		1
Cin	1		1	

- All are isolated 1.
- $$\begin{aligned}\text{Sum} &= AB'C' + A'BC' + A'B'C + ABC \\ &= C'(AB' + A'B) + C(A'B' + AB) \\ &= C'(A \oplus B) + C(A \oplus B)' \\ &= C'X + CX'; \text{ Let } X = A \oplus B \\ &= C \oplus X \\ &= C \oplus A \oplus B \\ &= A \oplus B \oplus Cin\end{aligned}$$


6-3 Design of a Full Adder

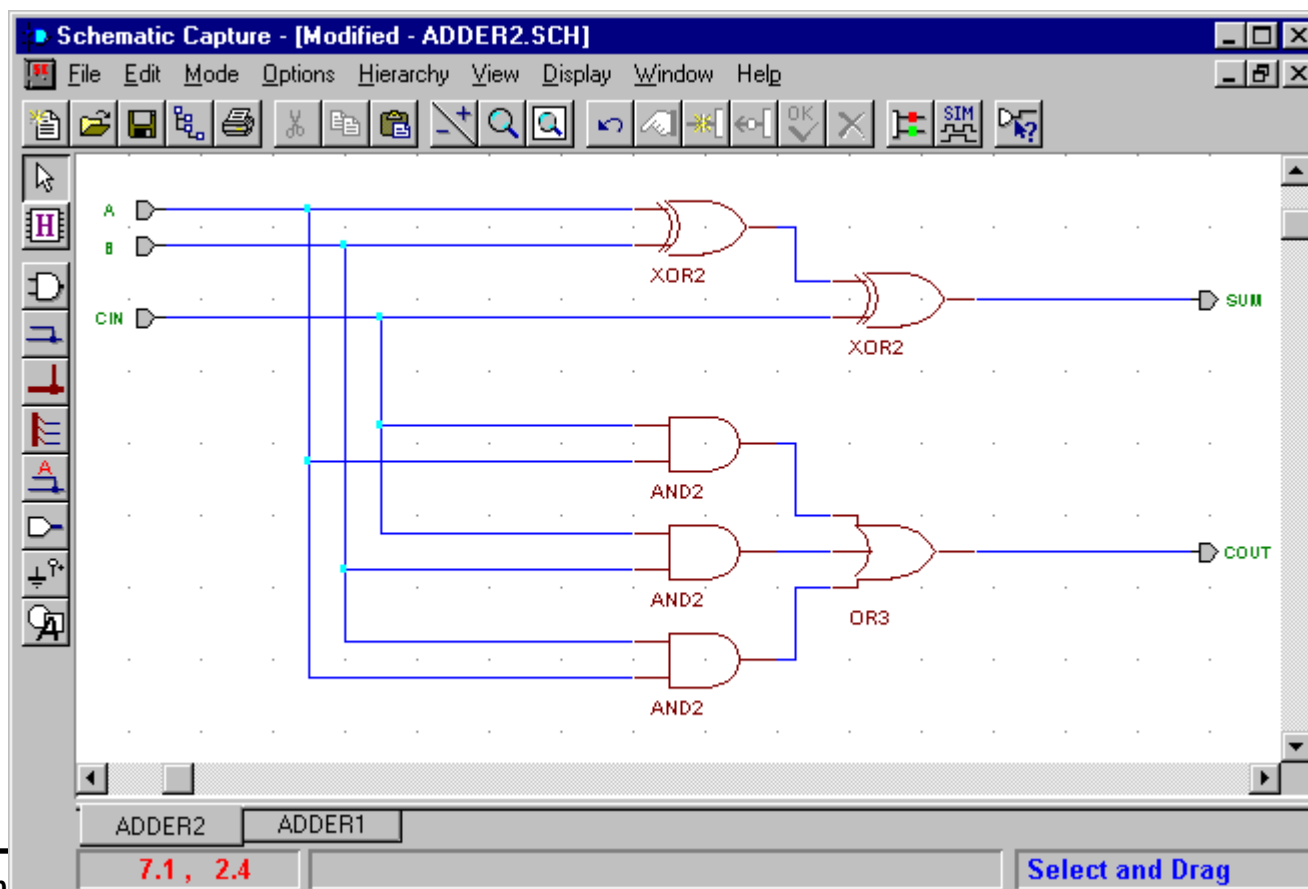 

6-3 Design of a Full Adder

- Block diagram of a Full Adder

Augend bit input	Addend bit input	Carry bit input	Sum bit output	Carry bit output
A	B	C_{IN}	S	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

6-4 4-bit Parallel Adder

- Suppose we want to add 2 four bit number like 1110+1011
- So we can follow the following procedure

$$\begin{array}{r} 11100 \leftarrow \text{Carry} \\ 1110 \\ + 1011 \\ \hline 11001 \leftarrow \text{Sum} \end{array}$$

6-4 4-bit Parallel Adder

C4 C3 C2 C1 C0 Carry

AUGEND A3 A2 A1 A0 A

ADDEND B3 B2 B1 B0 B

SUM S4 S3 S2 S1 S0 S


AUGEND A3 A2 A1 A0 ADDEND B3 B2 B1 B0

Generate sum bits, $S = A \oplus [B \oplus C_{in}]$

Generate carry bits, $C_{out} = A \cdot B + A \cdot C_{in} + B \cdot C_{in}$

 
6-4 4-bit Parallel Adder

Block diagram of a 4-bit parallel adder circuit using full adders.



 
6-4 4-bit Parallel Adder

- The most common parallel adder is a 4 bit device.
 - 4 interconnected FAs, and look-ahead carry circuits.
 - 7483A, 74LS83A, 74LS283, and 74HC283 are all four-bit parallel-adder chips.



 
6-4 4-bit Parallel Adder

- The A and B lines each represent 4 bit numbers to be added.
 - C_0 is the carry-in, C_4 is the carry-out, Σ is the sum.



 6-5 Cascading 4-bit Parallel Adder


Parallel adders may be cascaded together to add larger numbers, in this case two 8 bit numbers.



- **Subtraction in the 2's Complement System:**
- Subtraction using the 2's-complement system actually involves the operation of addition.
 - The number subtracted (subtrahend) is negated.
 - The result is added to the minuend.
 - The answer represents the difference.
- That is $A - B = A + (-B)$

 6-6 4-bit Parallel Subtractor

An adder can be used to perform subtraction by designing a way to take the 2's complement for subtraction—as shown.



6-7 4-bit Parallel Adder/Subtractor

4-bit Parallel adder/subtractor:

If Switch=0 then Adder

If Switch=1 then Subtractor

If S=0 then

First inputs are $A_3A_2A_1A_0$

Second inputs are $B_3B_2B_1B_0$ and $C_0=0$

So this is addition


If S= then

First inputs are $A_3A_2A_1A_0$

Second inputs are $B_3B_2B_1B_0$ and $C_0=1$

So this is Subtraction

6-7 4-bit Parallel Adder/Subtractor

 

6-8 BCD Adder

- What is BCD? Binary Coded Decimal

Decimal Number	BCD Code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

6-8 BCD Adder

BCD Addition:

- **Example 1:** $24+32=?$

- $24=0010\ 0100+$

- $32=0011\ 0010$

- $56=0101\ 0110$

- **Example 2:** $78+45=?$

- $78=0111\ 1000+$

- $45=0100\ 0101$

$? = 1011\ 1101$

$+ \quad +$

$0110\ 0110$

$1\ 0010\ 0011=123$

BCD Addition:

- When the sum of each decimal digit is less than 9, the operation is the same as normal binary addition.
- When the sum of each decimal digit is greater than 9, a binary 6 is added.
 - This will always cause a carry.

6-8 BCD Adder

A3A2A1A0

+

B3B2B1B0


S4S3S2S1S0

S4	S3	S2	S1	S0
0	0	1	1	1
0	1	0	0	0
0	1	0	0	1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0

- **Error Correction:**
 - Let us define X as a logic output that will be HIGH only when sum is greater than 9.
 - If we examine the above table, we can see that X will be HIGH for following conditions:
 - 1. When $S_4=1$ OR
 - 2. When $S_3=1$ and (either S_2 OR S_1 OR both are 1)
- So, **$X = S_4 + S_3.(S_2 + S_1)$**

- $A_3A_2A_1A_0$
- 0 0 0 0 if $X=0$
- 0 1 1 0 if $X=1$
- $A_3=A_0=0$
- $A_2=A_1=X$

6-8 BCD Adder

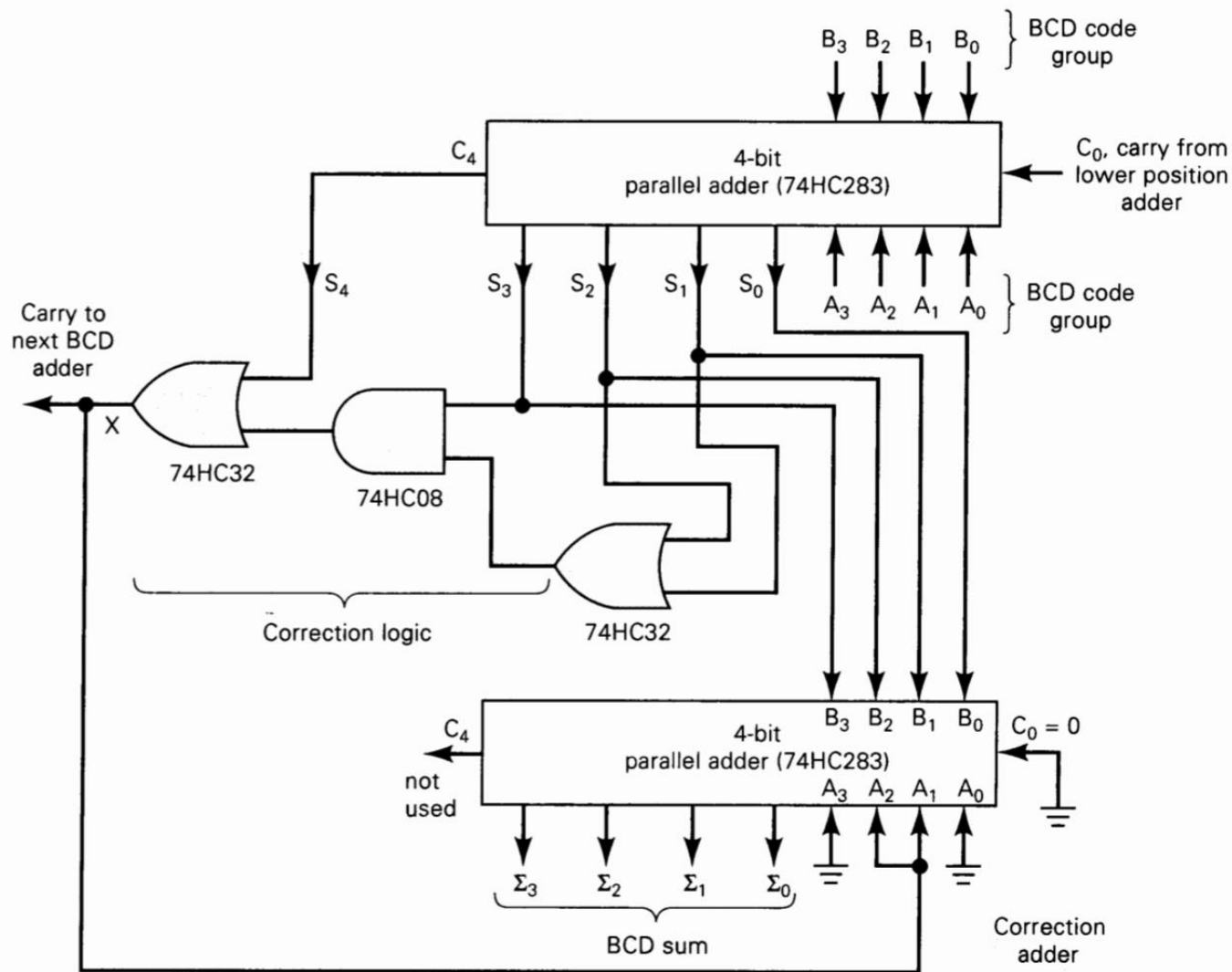

6-9 ALU Integrated Circuits

- ALUs can perform different arithmetic and logic functions as determined by a binary code on the function select inputs.


6-9 ALU Integrated Circuits

The 74LS382 (TTL) and HC382 (CMOS) is a typical device with 8 functions.

Function Table

S ₂	S ₁	S ₀	Operation	Comments
0	0	0	CLEAR	F ₃ F ₂ F ₁ F ₀ = 0000
0	0	1	B minus A	Needs C _N = 1
0	1	0	A minus B	
0	1	1	A plus B	Needs C _N = 0
1	0	0	A ⊕ B	Exclusive-OR
1	0	1	A + B	OR
1	1	0	AB	AND
1	1	1	PRESET	F ₃ F ₂ F ₁ F ₀ = 1111

 Notes: S inputs select operation.
OVR = 1 for signed-number overflow.



A = 4-bit input number
B = 4-bit input number
C_N = carry into LSB position
S = 3-bit operation select inputs

F = 4-bit output number
C_{N+4} = carry out of MSB position
OVR = overflow indicator

6-10 Expanding the ALU

- A single 74LS382 or 74HC382 operates on four-bit numbers. Two or more of these chips can be connected together to operate on larger numbers.

6-11 Model Question about this chapter

1. Draw the block diagram of 4 bit ALU chip (IC # 74382) and label the all inputs & outputs.
2. Describe 8(Eight) operations of the 4 bit ALU chip (IC # 74382) that perform by select inputs.
3. Design a BCD adder using IC # 7483 and basic gates if necessary. Briefly describe its operation.
4. What is BCD code? What is the problem in BCD addition? How can you overcome that?

6-11 Model Question about this chapter

5. Write down the truth tables of half adder and full adder. Design half adder and full adder using K-map or otherwise.
6. Briefly describe the operation of IC# 7483(4-bit parallel adder).
7. Design 4-bit Subtractor using IC # 7483(4-bit parallel adder).
8. Design a 4-bit parallel Adder/Subtractor using IC # 7483 and other logic gates if necessary. Briefly describe its operation.

6-11 Model Question about this chapter

9. Design 8-bit parallel Adder using IC # 7483(4-bit parallel adder).
10. Design 8-bit parallel Subtractor using IC # 7483(4-bit parallel adder).
11. Design 8 bit ALU chip using 4 bit ALU chips (IC # 74382) and label the all inputs & outputs.
12. Describe 8(Eight) operations of the 8 bit ALU chip that perform by select inputs.