



UNIVERSITY OF ASIA PACIFIC

Department of Computer Science & Engineering

Course Title : Digital Logic & System Design Lab

Course Code : CSE 210

Experiment No. : 04

Experiment Name :

- a) Design 1 bit Half Adder and Full Adder
- b) Test and verify the 4-bit parallel Adder(IC # 7483)
- c) Design Subtractor using IC # 7483
- d) Adder + Subtractor
- e) Design a 4 bit adder-subtractor with full adders.

Date of Performance : 08-02-2022

Date of Submission : 14-02-2022

Submitted by:

Name : Sheikh Nafez Sadnan

Reg. No. : 20101106

Roll No. : 106

Section : B₍₂₎

Submitted To:

Shammi Akhtar

Assistant Professor

Department of CSE

University of Asia Pacific

Problem Statement:

- a) Design 1 bit Half Adder and Full Adder
- b) Test and verify the 4-bit parallel Adder(IC # 7483)
- c) Design Subtractor using IC # 7483
- d) Adder + Subtractor
- e) Design a 4 bit adder-subtractor with full adders.

Instruments (Used in This Experiment):

- i. XOR GATE (IC-7486)
- ii. AND GATE (IC-7408)
- iii. OR GATE (IC-7432)
- iv. NOT GATE (IC-7404)
- v. IC-7483
- vi. Logic Switch
- vii. Logic Display

a) Design 1 bit Half Adder and Full Adder

HALF ADDER :

Truth Table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Logic Expression:

$$\text{Sum} = A'B + AB' = A \oplus B$$


$$\text{Carry} = AB$$

Circuit Diagram:


For A=0, B=0

 


For A=0, B=1

 

For A=1, B=0

 

For A=1, B=1

 

FULL ADDER :

Truth Table:


A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Logic Expression:


$$\begin{aligned}
 \text{Sum} &= A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin} \\
 &= A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin} + A' B' \text{Cin} \\
 &= \text{Cin}' (A' B + A B') + \text{Cin} (A \oplus B)' \\
 &= \text{Cin}' X + \text{Cin} X' \quad [\text{Let } A \oplus B = X] \\
 &= \text{Cin} \oplus X \\
 &= \text{Cin} \oplus A \oplus B \\
 &= A \oplus B \oplus \text{Cin}
 \end{aligned}$$

$$\begin{aligned}
 \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= \text{Cin} (A' B + A B') + A B (\text{Cin}' + \text{Cin}) \\
 &= \text{Cin} (A \oplus B) + A B \cdot 1 \\
 &= \text{Cin} (A \oplus B) + A B
 \end{aligned}$$


Circuit Diagram: For A=0, B=0, Cin=0

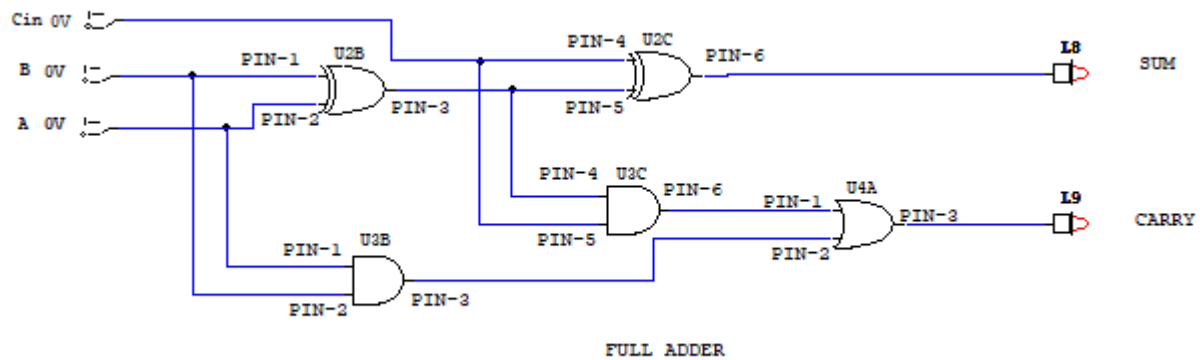


For A=0, B=0, Cin=1

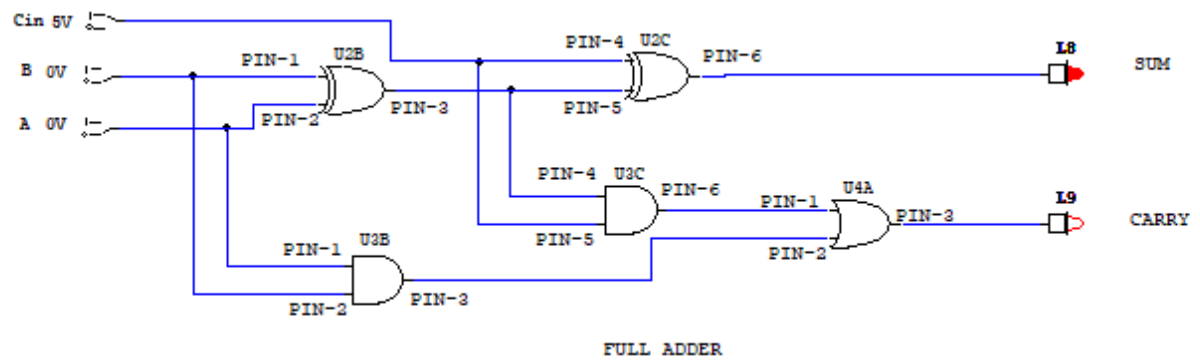


For A=0, B=1, Cin=0

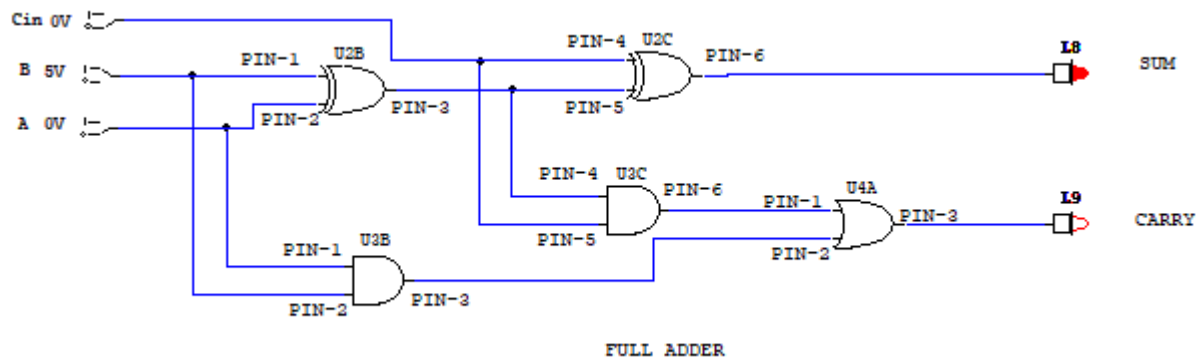


For A=0, B=1, Cin=1

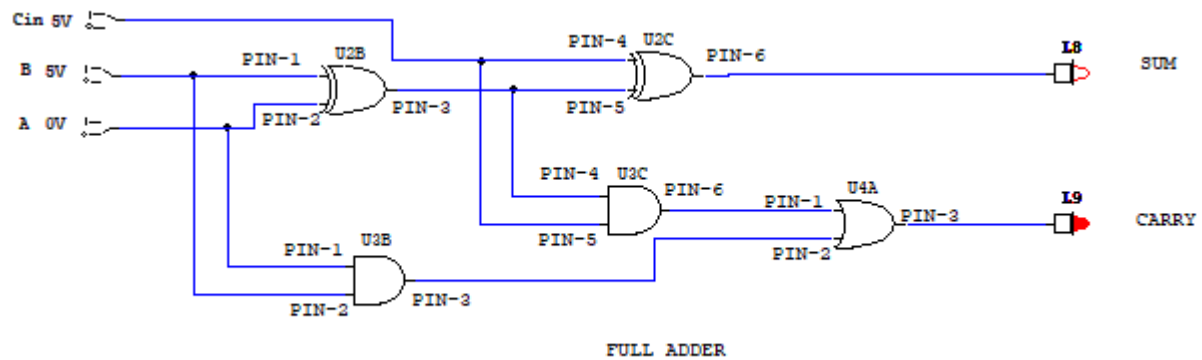


For A=1, B=0, Cin=0

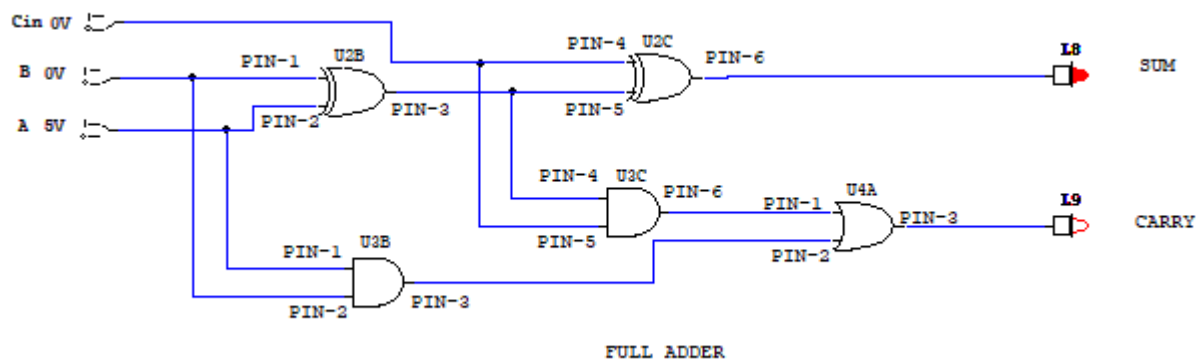


For A=1, B=0, Cin=1

 

For A=1, B=1, Cin=0

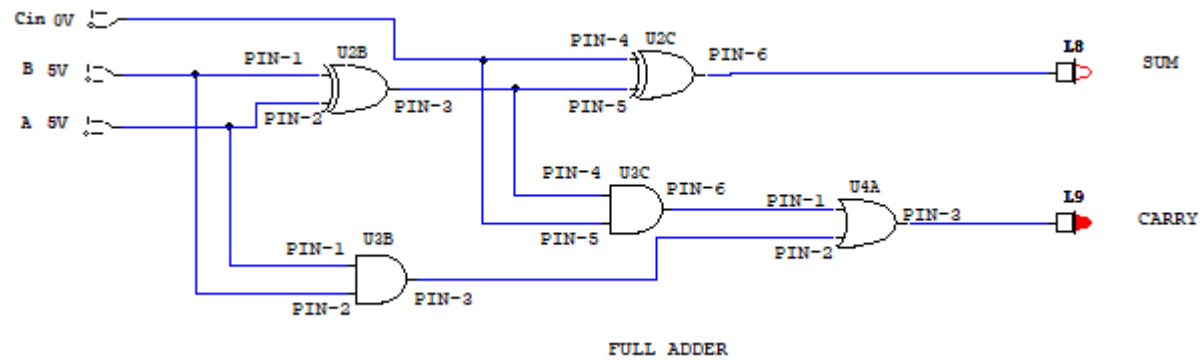

For A=1, B=1, Cin=1

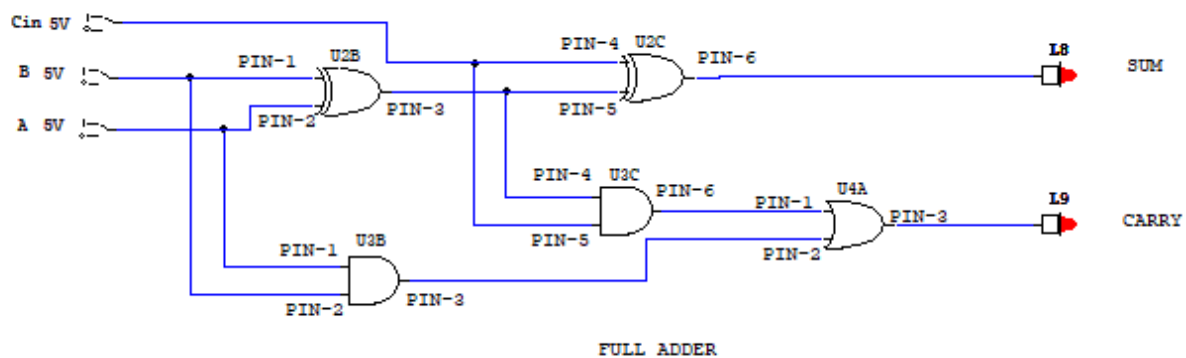

b) Test and verify the 4-bit parallel Adder(IC # 7483)

Adder Calculation:

A = 15 = 1111 (A4 A3 A2 A1)

B = 14 = 1110 (B4 B3 B2 B1)


Sum = 29 = 11101 (Cout S4 S3 S2 S1)

Circuit Diagram:

A = 15 = 1111

B = 14 = 1110

Sum = 29 = 11101

 

c) Design Subtractor using IC # 7483

Subtractor Calculation:

$$A = 15 = 1111 \text{ (A4 A3 A2 A1)}$$

$$B = 14 = 1110 \text{ (B4 B3 B2 B1)}$$

$$\text{So, } -B = -14 = 0010 \text{ (B4 B3 B2 B1)}$$

In Subtraction we use negative value's 2's compliment. Here we add +15 that's mean 1111 and -14 that's mean 0010.

So,

$$A = 15 = 1111 \text{ (A4 A3 A2 A1)}$$

$$-B = -14 = 0010 \text{ (B4 B3 B2 B1)}$$

$$\text{Subtraction} = 1 = 10001 \text{ (Cout S4 S3 S2 S1)}$$

But when we input value in Subtractor we put $A = 1111$ and $B = 1110$.

Circuit Diagram:


Here consider that,

$$A = 15 = 1111$$


$$B = 14 = 1110$$

$$\text{Subtraction} = 1 = 10001$$

(using NOT gate)

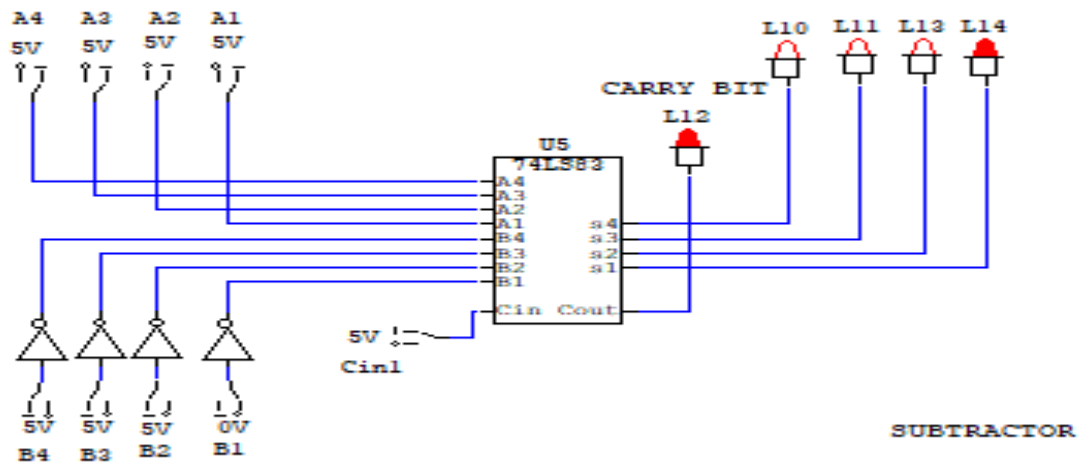

(using XOR gate)

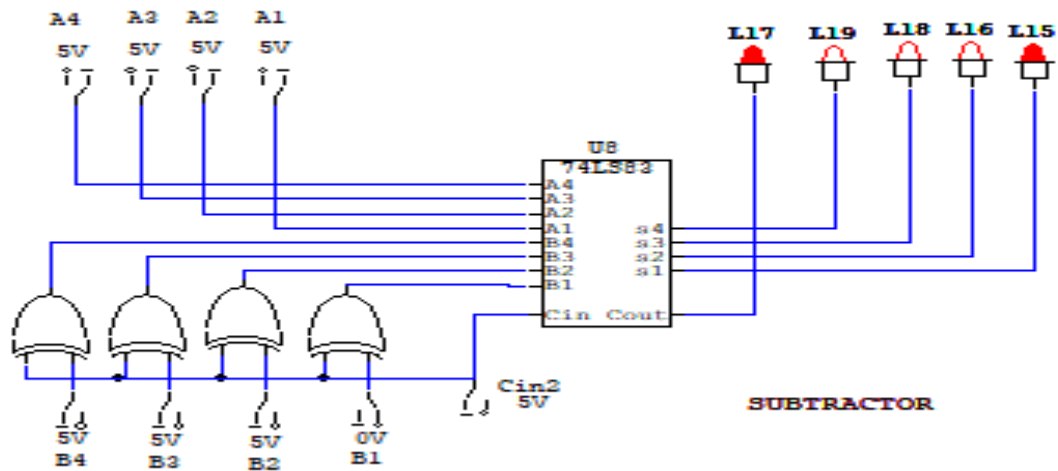

d) Adder + Subtractor

Calculation :

For Adder,

$$A = 15 = 1111$$

$$B = 14 = 1110$$

$$\text{Sum} = 29 = 11101$$

For Subtractor,

$$A = 15 = 1111$$

$$B = 14 = 1110$$


$$= 0001 \text{ [1's complement of B]}$$

+1


$$= 0010 \text{ [2's complement of B]}$$

$$\text{So, Subtraction} = 10001$$

Circuit Diagram: (FOR ADDER)

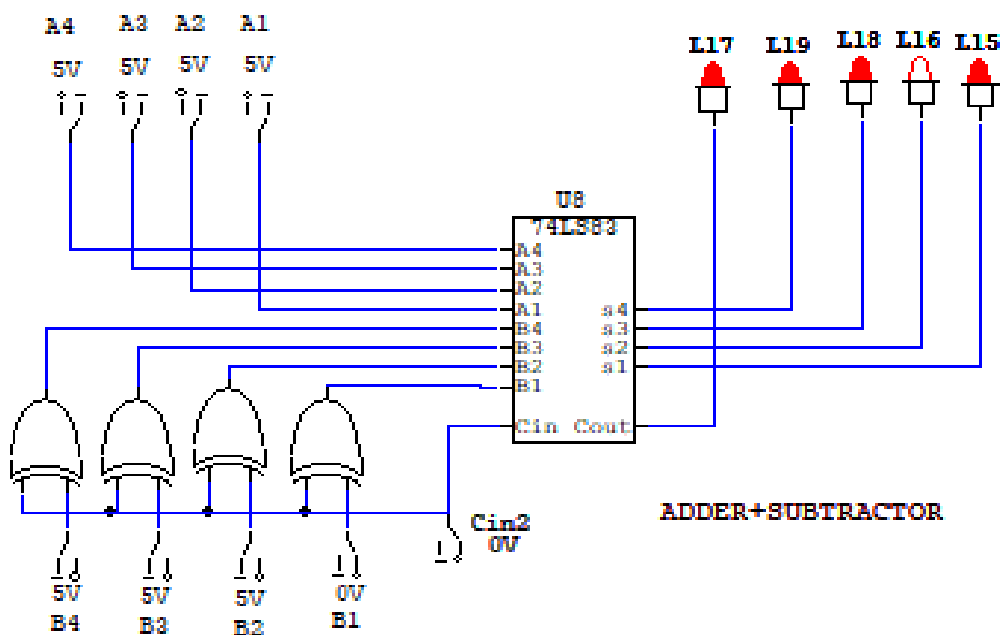

(FOR SUBTRACTOR)

 

e) Design a 4 bit adder-subtractor with full adders


FOR ADDITION OPERATION:

A = 15 = 1111 (A4 A3 A2 A1)

B = 14 = 1110 (B4 B3 B2 B1)

Sum = 29 = 11101 (Cout S4 S3 S2 S1)

Circuit Diagram:

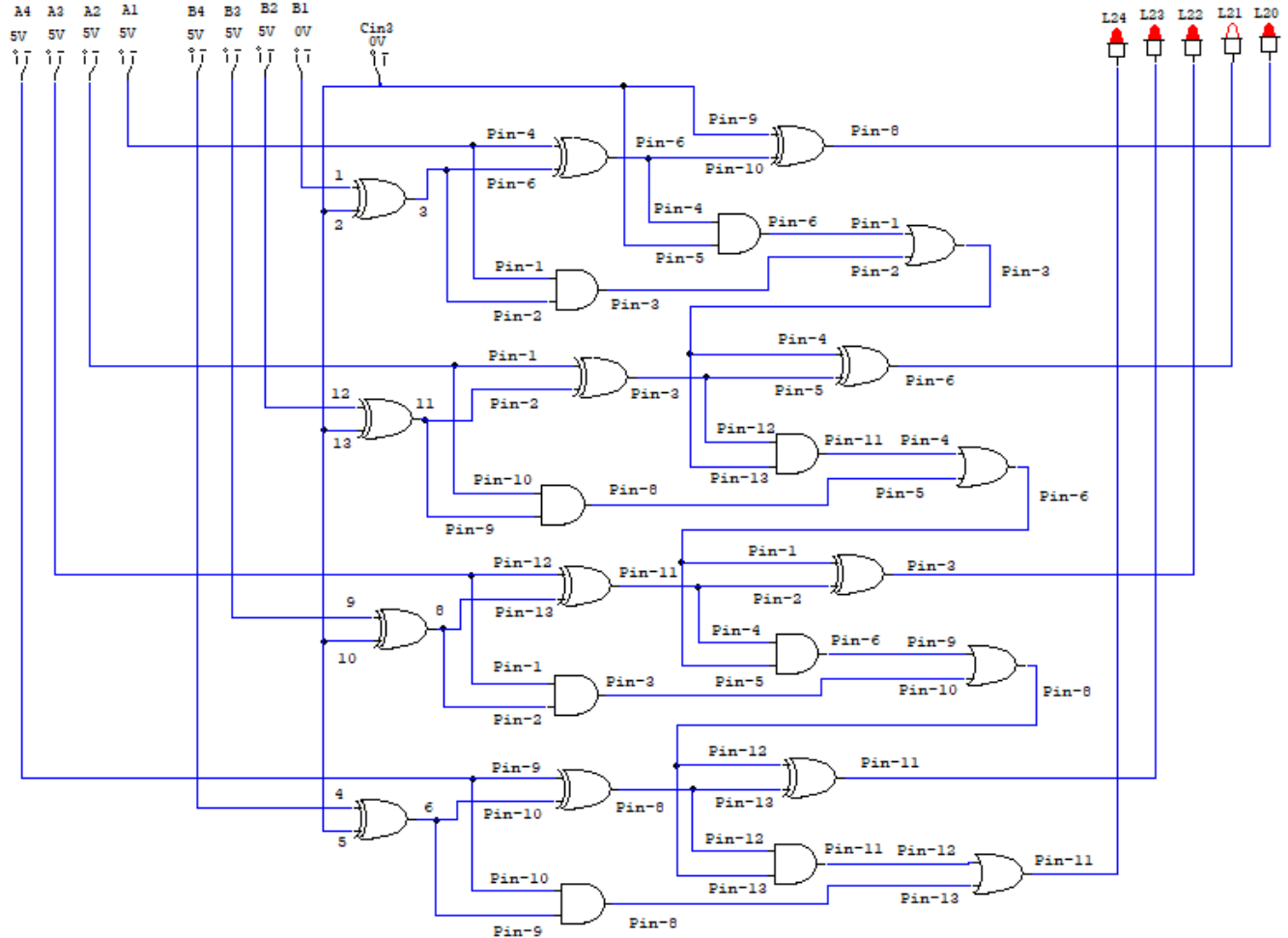

4 – bit example of Adder and Subtractor:


For addition operation:

$$A = 12 = 1100 \quad (A_4 A_3 A_2 A_1)$$

$$B = 11 = 1011 \quad (B_4 B_3 B_2 B_1)$$

$$\text{Sum} = 23 = 10111 \quad (\text{Cout } S_4 S_3 S_2 S_1)$$

Circuit Diagram:

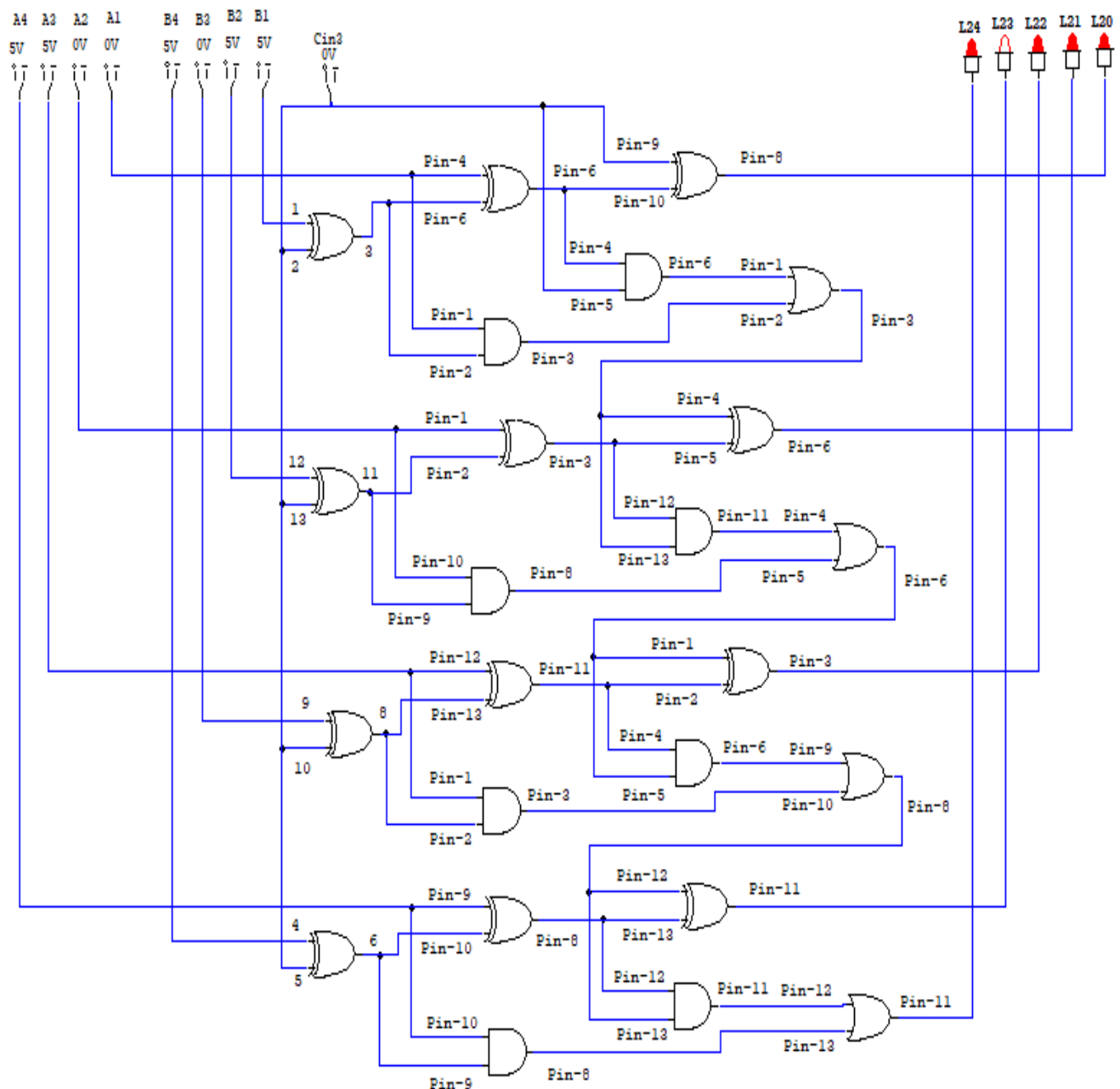


For subtraction operation:

$$\begin{aligned}
 A &= 12 = 1100 \\
 B &= 11 = 1011 \\
 &= 0100 \text{ [1's complement of B]} \\
 &\quad +1 \\
 &= 0101 \text{ [2's complement of B]}
 \end{aligned}$$

So, Subtraction = 10001

Circuit Diagram:

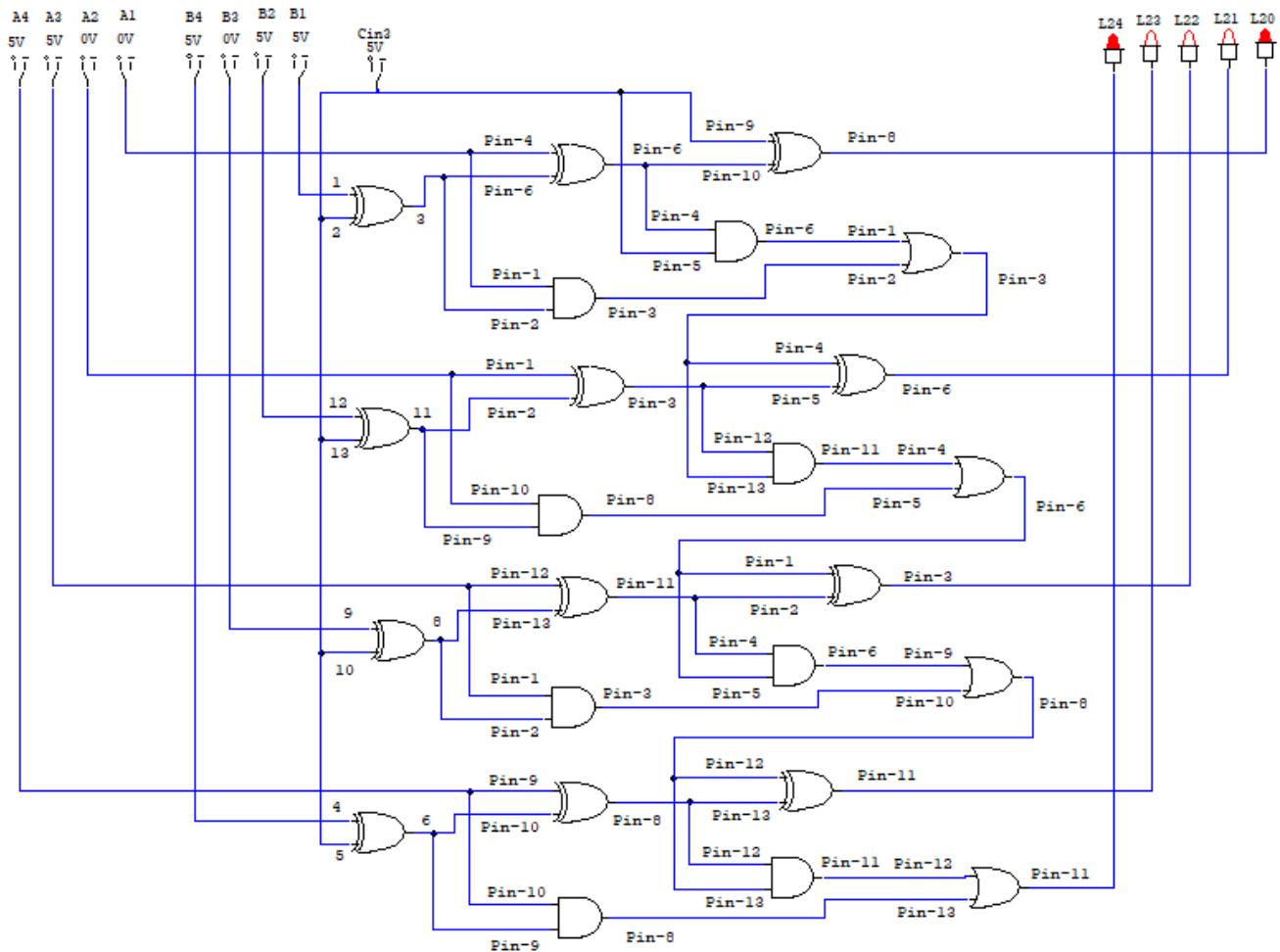

Discussion : In this experiment we learned about half adder & full adder. We also discussed about 4 bit parallel adder. We have verified 4-bit parallel adder using IC#7483. We also designed subtractor using IC#7483 and verified it. We designed adder+subtractor and a 4-bit example of adder and subtractor using full adder. Security issues were strictly maintained during the experiment.