

Chapter 5: **Flip-Flops and Related Devices**


Prof. Dr. Aloke Kumar Saha
Professor
Department of CSE
University of Asia Pacific (UAP)

Chapter 5 Objectives

- *Selected areas covered in this chapter:*
 - Basic structures of flip-flops.
 - Constructing/analyzing operation of latch made from NAND or NOR gates.
 - Differences of synchronous/asynchronous systems.
 - Operation of edge-triggered flip-flops.
 - Constructing/analyzing operation of clocked S-R flip-flop.
 - Constructing/analyzing operation of clocked J-K flip-flop.
 - Constructing/analyzing operation of clocked D flip-flop.
 - Basic operation of asynchronous inputs J-K flip-flop.
 - Counter and frequency division.
 - MOD 8 Up Counter, Down Counter, Up/Down Counter
 - MOD 16 Up Counter, Down Counter, Up/Down Counter

Chapter 5 Introduction


 
- The most important memory element is the **flip-flop (FF)**—made up of an assembly of logic gates.



The flip-flop is known by other names, including *latch* and *bistable multivibrator*.

  
5-1 NAND Gate Latch

- The **NAND** gate latch or simply latch is a basic FF.
 - Inputs are *SET* and *CLEAR (RESET)*.
- Inputs are active-LOW—output will change when the input is pulsed LOW.
 - When the latch is set: $Q = 1$ and $\bar{Q} = 0$
 - When the latch is clear or reset: $Q = 0$ and $\bar{Q} = 1$



 5-1 NAND Gate Latch – Setting the Latch (FF)



- Pulsing the SET input to the 0 state...
 - (a) $Q = 0$ prior to SET pulse.
 - (b) $Q = 1$ prior to SET pulse.



In both cases, Q ends up HIGH.

  5-1 NAND Gate Latch – Resetting the Latch (FF)



- Pulsing RESET LOW when...
 - (a) $Q = 0$ prior to the RESET pulse.
 - (b) $Q = 1$ prior to the RESET pulse.



In each case, Q ends up LOW.

  5-1 NAND Gate Latch – Alternate Representations

NAND latch equivalent representations and simplified block diagram.




Set	Reset	Output(Q)
0	0	Invalid
0	1	1
1	0	0
1	1	No Change

5-1 NAND Gate Latch - Summary

- Summary of the **NAND** latch:
 - **SET = 1, RESET = 1**—Normal resting state, outputs remain in state they were in prior to input.
 - **SET = 0, RESET = 1**—Output will go to $Q = 1$ and remains there, even after SET returns HIGH.
 - Called *setting* the latch.
 - **SET = 1, RESET = 0**—Will produce $Q = 0$ LOW and remains there, even after RESET returns HIGH.
 - Called *clearing* or *resetting* the latch.
 - **SET = 0, RESET = 0**—Tries to set and clear the latch at the same time, and produces $Q = \bar{Q} = 1$.
 - Output is unpredictable, and this input condition should not be used.


5-1 NAND Gate Latch

- Waveform diagram of NAND Latch

 

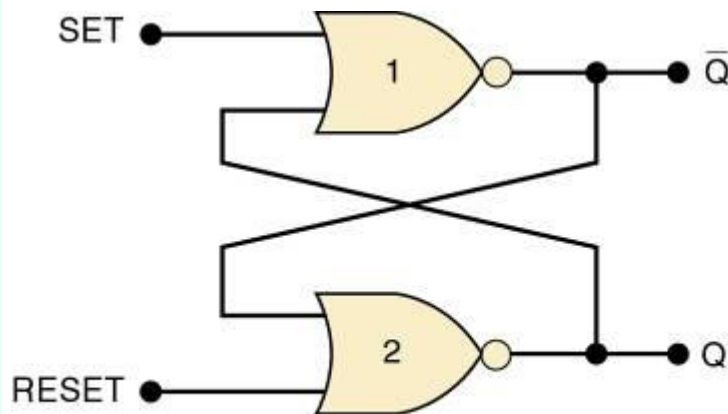
5-2 NOR Gate Latch

- Two cross-coupled **NOR** gates can be used as a **NOR** gate latch—similar to the **NAND** latch.
 - The **Q** and \bar{Q} outputs are reversed.



Set	Reset	Output
0	0	No change
1	0	Q = 1
0	1	Q = 0
1	1	Invalid*

*Produces $Q = \bar{Q} = 0$.

 


The SET and RESET inputs are active-HIGH.
Output will change when the input is pulsed HIGH.

5-2 NOR Gate Latch - Summary

- Summary of the **NOR** latch:
 - **SET = 0, RESET = 0**—Normal resting state, No effect on output state.
 - **SET = 1, RESET = 0**—will always set $Q = 1$, where it remains even after SET returns to 0.
 - **SET = 0, RESET = 1**—will always clear $Q = 0$, where it remains even after RESET returns to 0.
 - **SET = 1, RESET = 1**—Tries to set and reset the latch at the same time, and produces $Q = \overline{Q} = 0$.
 - Output is unpredictable, and this input condition should not be used.

5-2 NOR Gate Latch

- Waveform diagram of NOR Latch

 


5-3 Clock Signals and Clocked Flip-Flops

- Digital systems can operate either *asynchronously* or *synchronously*.
 - **Asynchronous system**—outputs can change state at any time the input(s) change.
 - **Synchronous system**—output can change state only at a specific time in the clock cycle.

5-3 Clock Signals and Clocked Flip-Flops

- The clock signal is a rectangular pulse train or square wave.
 - Positive going transition (PGT)—clock pulse goes from 0 to 1.
 - Negative going transition (NGT)—clock pulse goes from 1 to 0.


Transitions are also called *edges*.

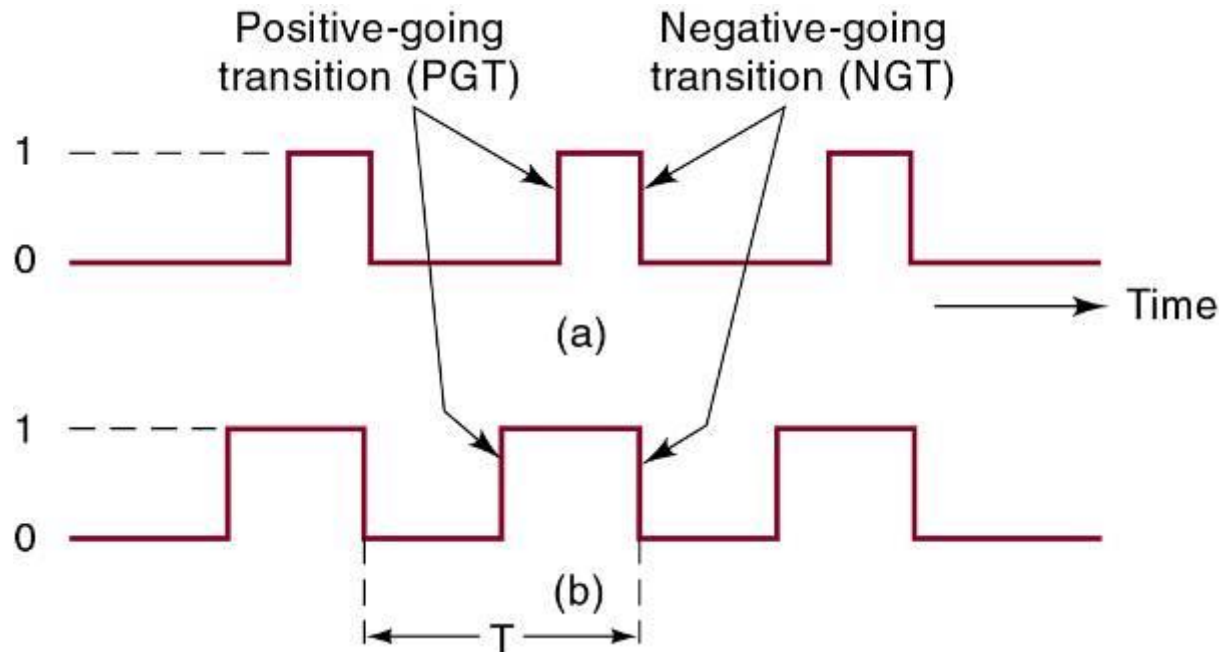

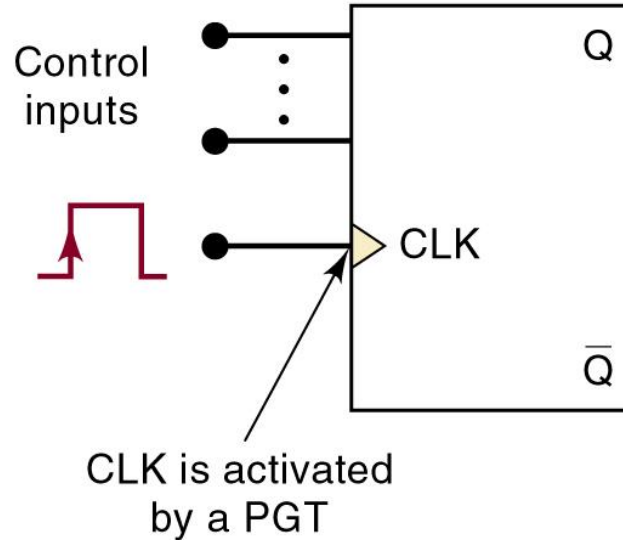
5-3 Clock Signals and Clocked Flip-Flops

- Clocked FFs change state on one or the other clock transitions.
 - Clock inputs are labeled CLK, CK, or CP.

A small triangle at the CLK input indicates that the input is activated with a PGT.





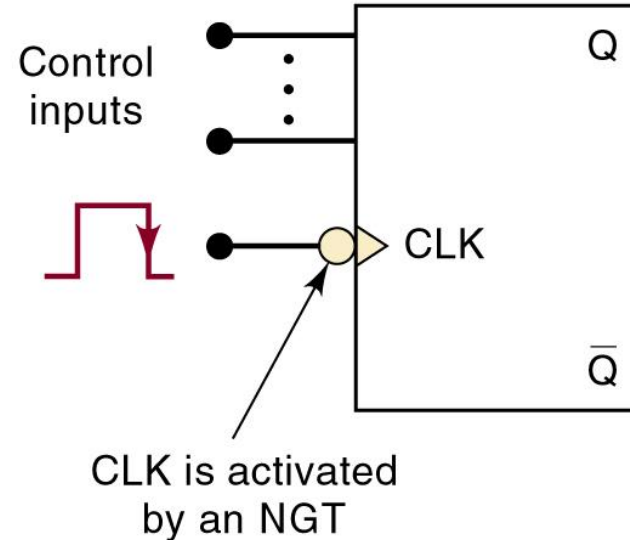A bubble and a triangle indicates that the CLK input is activated with a NGT.



 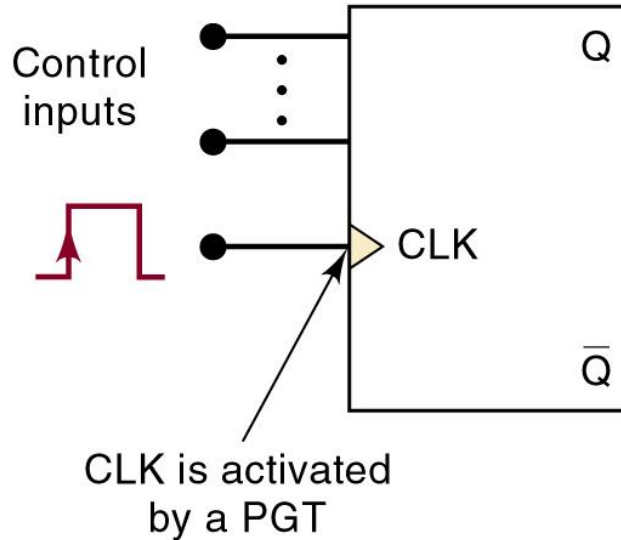5-3 Clock Signals and Clocked Flip-Flops

- Control inputs have an effect on the output only at the active clock transition (NGT or PGT)—also called synchronous control inputs.
 - The control inputs get the outputs ready to change, but the change is not triggered until the CLK edge.




5-4 Clocked S-R Flip-Flop

- The S and R inputs are synchronous *control* inputs, which control the state the FF will go to when the clock pulse occurs.
 - The CLK input is the **trigger** input that causes the FF to change states according to the S and R inputs.
- SET-RESET (or SET-CLEAR) FF will change states at positive- or negative-going clock edges.

 5-4 Clocked S-R Flip-Flop

A clocked S-R flip-flop triggered by the positive-going edge of the clock signal.




Inputs			Output
S	R	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous

Q_0 is output level prior to ↑ of CLK.
↓ of CLK produces no change in Q.

The S and R inputs control the state of the FF in the same manner as described earlier for the NOR gate latch, but the FF does *not* respond to these inputs *until* the occurrence of the PGT of the clock signal.

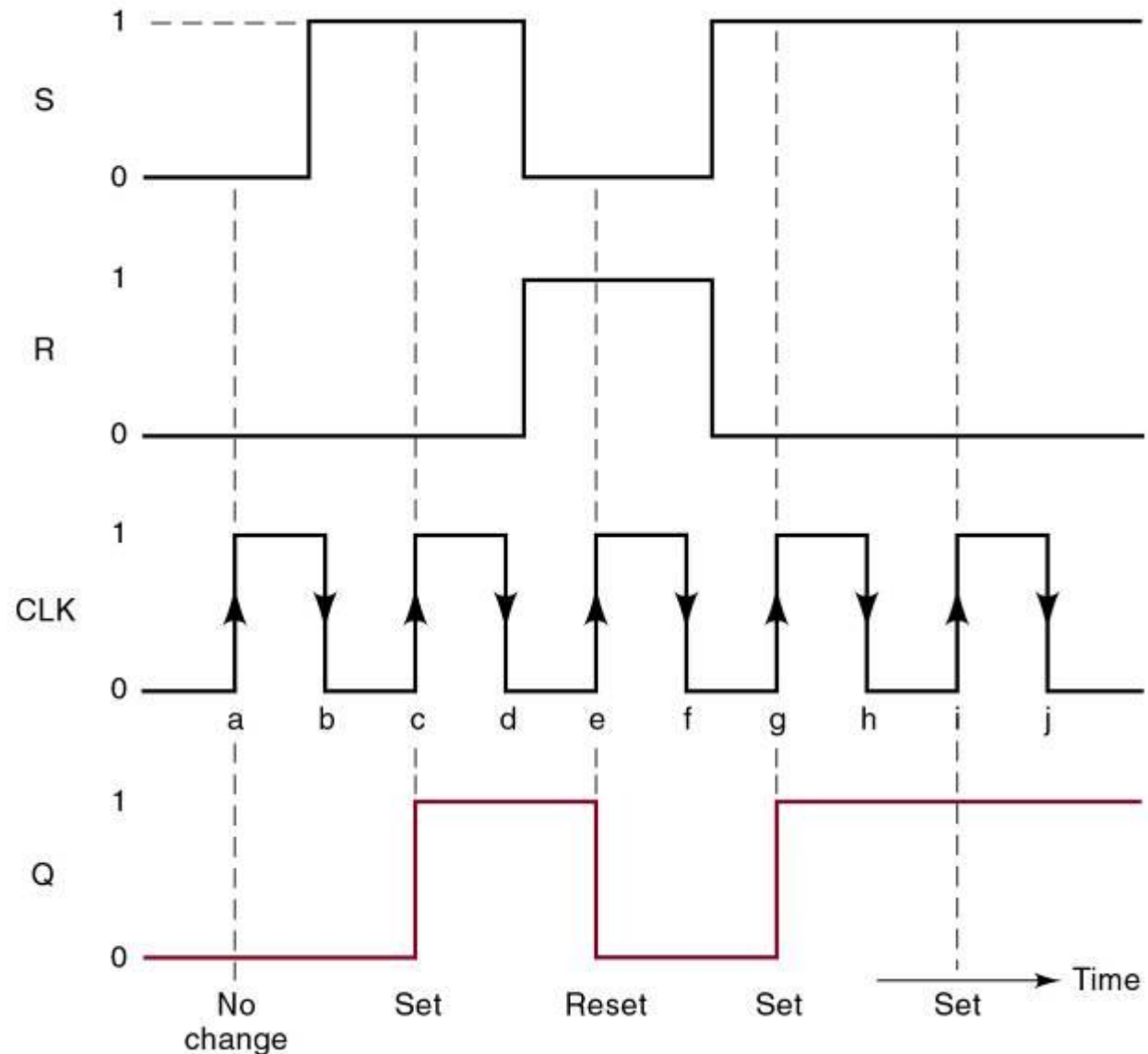
5-4 Clocked S-R Flip-Flop

Waveforms of the operation of a clocked S-R flip-flop triggered by the positive-going edge of a clock pulse.



 5-4 Clocked S-R Flip-Flop


A clocked S-R flip-flop triggered by the negative-going edge of the clock signal.



Inputs			Output
S	R	CLK	Q
0	0	↓	Q_0 (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Ambiguous

Both positive-edge and negative-edge triggering FFs are used in digital systems.


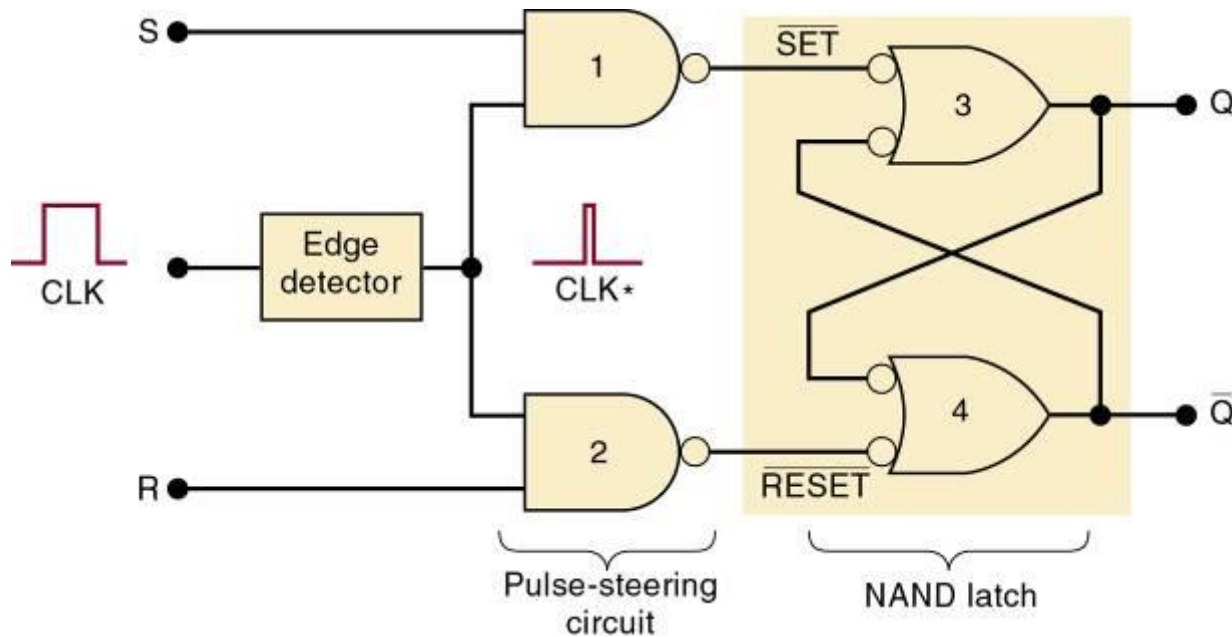
5-4 Clocked S-R Flip-Flop – Internal Circuitry





- An edge-triggered S-R flip-flop circuit features:
 - A basic **NAND** gate latch formed by **NAND-3** and **NAND-4**.
 - A **pulse-steering circuit** formed by **NAND-1** and **NAND-2**.
 - An **edge-detector circuit**.

  5-4 Clocked S-R Flip-Flop – Internal Circuitry

- Implementation of edge-detector circuits used in edge-triggered flip-flops:
 - (a) PGT; (b) NGT.



(a)

  

(b)


The duration of the CLK^* pulses is typically 2–5 ns.

5-5 Clocked J-K Flip-Flop

- Operates like the S-R FF.
 - J is SET, K is CLEAR.
- When J and K are both HIGH, output is toggled to the opposite state.
 - May be positive going or negative going clock trigger.
- Much more versatile than the S-R flip-flop, as it has no ambiguous states.
 - Has the ability to do everything the S-R FF does, plus operates in toggle mode.

 
5-5 Clocked J-K Flip-Flop – Internal Circuitry

- Internal Circuit of Clocked J-K Flip-Flop




5-5 Clocked J-K Flip-Flop

- Block Diagram Clocked J-K Flip-Flop

 

 
5-5 Clocked J-K Flip-Flop – Internal Circuitry

- The internal circuitry of an edge-triggered J-K flip-flop contains the same three sections as the edge-triggered S-R flip-flop.




 5-5 Clocked J-K Flip-Flop

Clocked J-K flip-flop that responds only to the positive edge of the clock.




J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	\bar{Q}_0 (toggles)

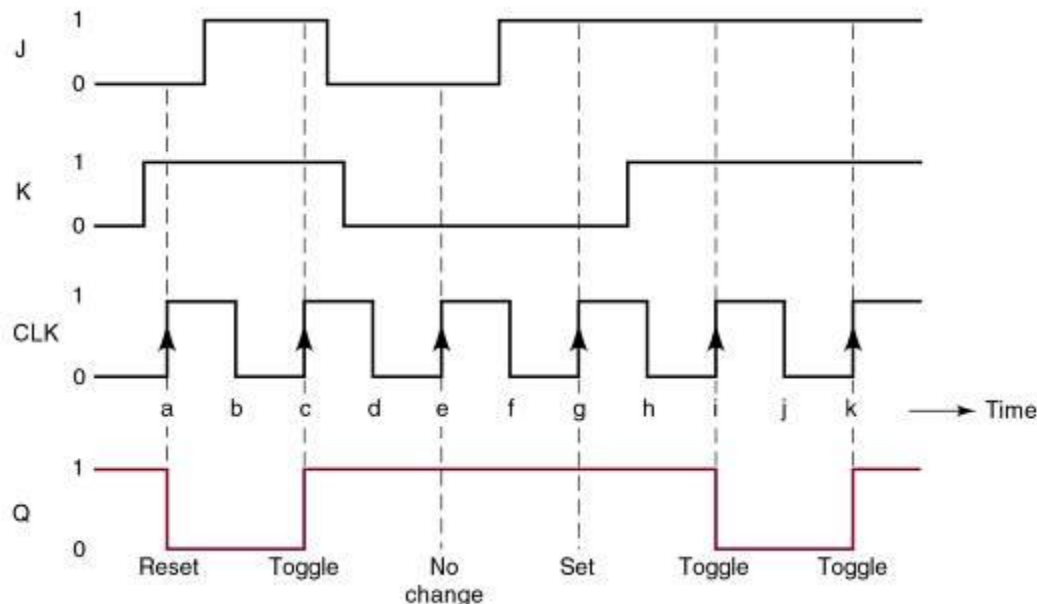

 5-5 Clocked J-K Flip-Flop

Clocked J-K flip-flop that responds only to the negative edge of the clock.




J	K	CLK	Q
0	0	↓	Q_0 (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	$\overline{Q_0}$ (toggles)

5-6 Clocked D Flip-Flop

- One data input—output changes to the value of the input at either the positive- or negative-going clock trigger.
- May be implemented with a J-K FF by tying the J input to the K input through an inverter.
- Useful for parallel data transfer.


 
5-6 Clocked D Flip-Flop

- Internal Circuit of Clocked D Flip-Flop



  5-6 Clocked D Flip-Flop


D flip-flop that triggers only on positive-going transitions.



 5-7 Clocked J-K to D Flip-Flop - Implementation

- A clocked D flip-flop is implemented by adding a single INVERTER to the clocked J-K flip-flop.
 - The same can be done to convert a S-R flip-flop to a D flip-flop.

Edge-triggered D flip-flop implementation from a J-K flip-flop.




5-8 Asynchronous Inputs

- Inputs that depend on the clock are synchronous.
- Most clocked FFs have asynchronous inputs that do not depend on the clock.
 - Labels PRE & CLR are used for asynchronous inputs.
- Active-LOW asynchronous inputs will have a bar over the labels and inversion bubbles.
- If the asynchronous inputs are not used they will be tied to their inactive state.

 5-8 Asynchronous Inputs

Clocked J-K flip-flop with asynchronous inputs.




J	K	Clk	$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	Q
0	0	↓	1	1	Q (no change)
0	1	↓	1	1	0 (Synch reset)
1	0	↓	1	1	1 (Synch set)
1	1	↓	1	1	\bar{Q} (Synch toggle)
x	x	x	1	1	Q (no change)
x	x	x	1	0	0 (asynch clear)
x	x	x	0	1	1 (asynch preset)
x	x	x	0	0	(Invalid)

● 5-8 Asynchronous Inputs - Designations


- IC manufacturers do not agree on nomenclature for asynchronous inputs.
 - The most common designations are *PRE* (PRESET) and *CLR* (CLEAR).
 - Clearly distinguished from synchronous SET & RESET.
 - Labels such as *S-D* (direct SET) and *R-D* (direct RESET) are also used.

 5-8 Asynchronous Inputs

A J-K FF that responds to a NGT on its clock input and has active-LOW asynchronous inputs.



Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{\text{PRE}} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{\text{CLR}} = 0$
f	$\overline{\text{CLR}}$ overrides the NGT of CLK
g	Synchronous toggle

 

5-9 Flip-Flop Timing Considerations - Parameters

- Important timing parameters:
 - Setup and hold times
 - **Propagation delay**—time for a signal at the input to be shown at the output. (t_{PLH} and t_{PHL})
 - **Maximum clocking frequency**—Highest clock frequency that will give a reliable output. (f_{MAX})
 - **Clock pulse HIGH and LOW times**—minimum clock-time between HIGH/LOW changes. ($t_w(L)$; $t_w(H)$)
 - **Asynchronous Active Pulse Width**—time the clock must HIGH before going LOW, and LOW before going HIGH.
 - **Clock transition times**—maximum time for clock transitions,
 - Less than 50 ns for TTL ; 200 ns for CMOS

5-10 Flip-Flop Applications

- Frequency Division
- Counting



5-11 Frequency Division and Counting

J-K flip-flops wired as a three-bit binary counter (MOD-8).

Each FF divides the input frequency by 2.

Output frequency is 1/8 of the input (clock) frequency.

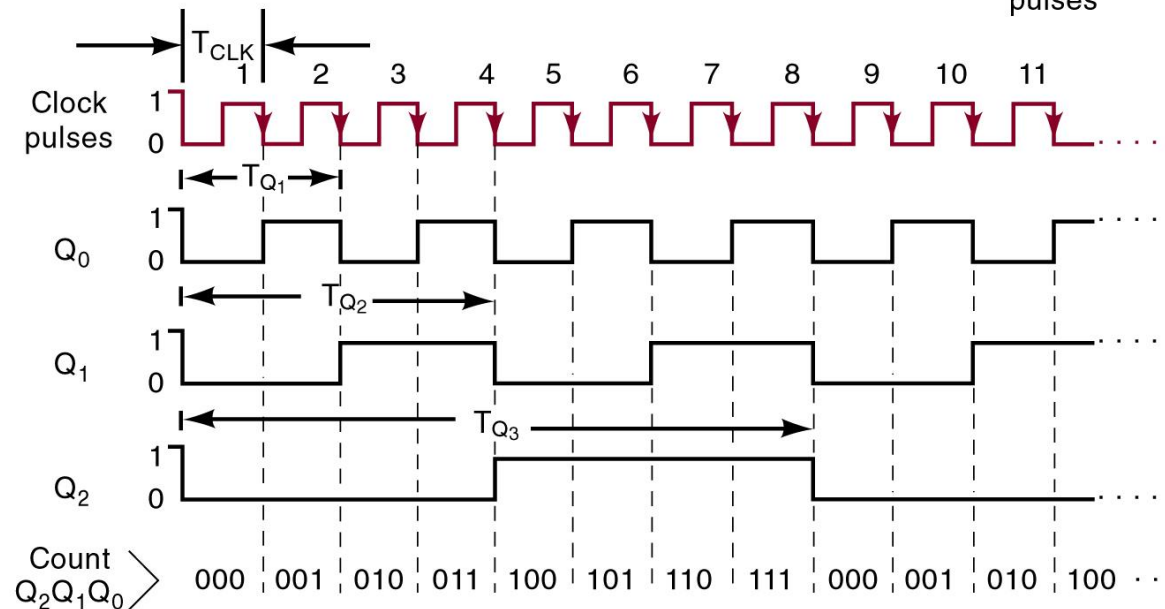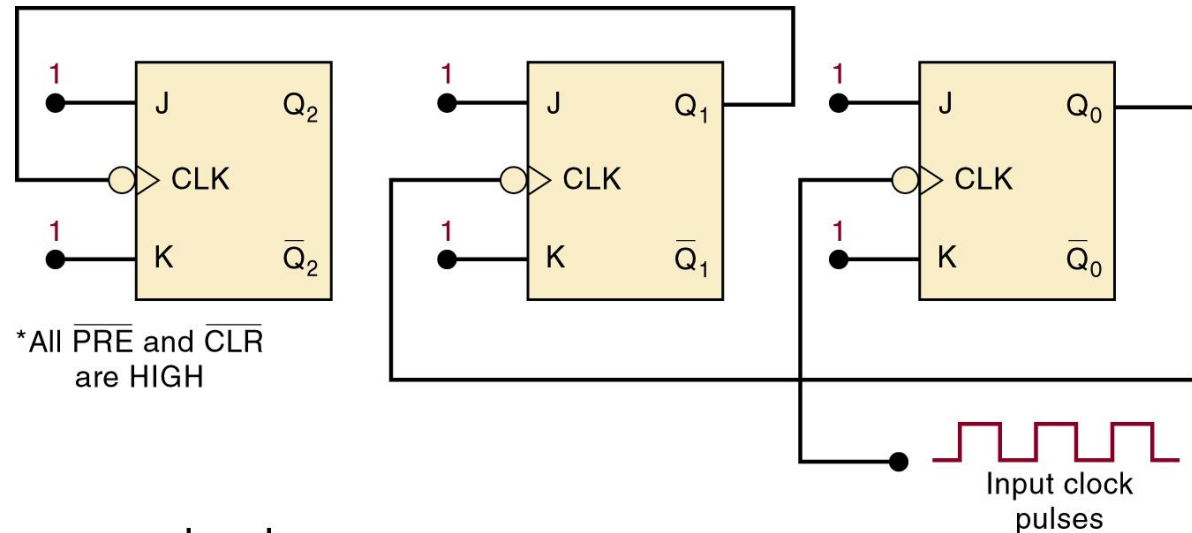A fourth FF would make the frequency 1/16 of the clock.





5-11 Frequency Division and Counting

J-K flip-flops wired as a three-bit binary counter (MOD-8).

This circuit also acts as a binary counter.

Outputs will count from 000 to 111 or 0 to 7.

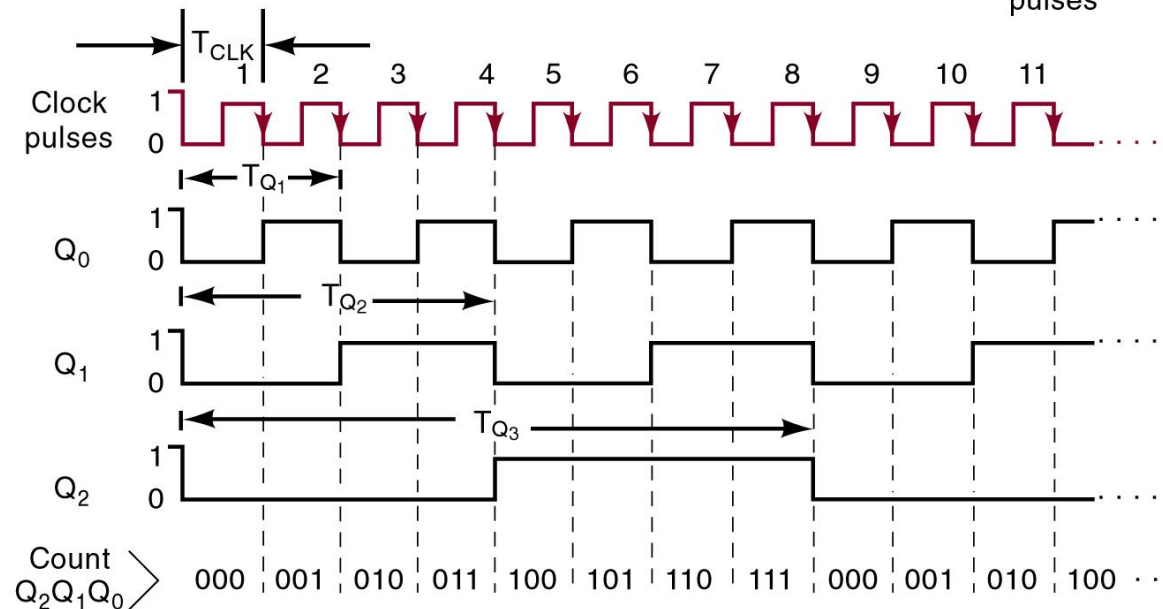 The number of states possible in a counter is the modulus or MOD number.




5-11 Frequency Division and Counting

A MOD-8 (2^3) counter.


If another FF is added it would become a MOD-16 (2^4) counter.

2^2	2^1	2^0	
Q_2	Q_1	Q_0	
0	0	0	Before applying clock pulses
0	0	1	After pulse #1
0	1	0	After pulse #2
0	1	1	After pulse #3
1	0	0	After pulse #4
1	0	1	After pulse #5
1	1	0	After pulse #6
1	1	1	After pulse #7
0	0	0	After pulse #8 recycles to 000
0	0	1	After pulse #9
0	1	0	After pulse #10
0	1	1	After pulse #11
.	.	.	.
.	.	.	.
.	.	.	.

 

5-11 Frequency Division and Counting


- Internal Circuit of MOD 8 Up Counter

 

©Elprocus.com

5-11 Frequency Division and Counting


- Internal Circuit of MOD 16 Up Counter

 


©Elprocus.com

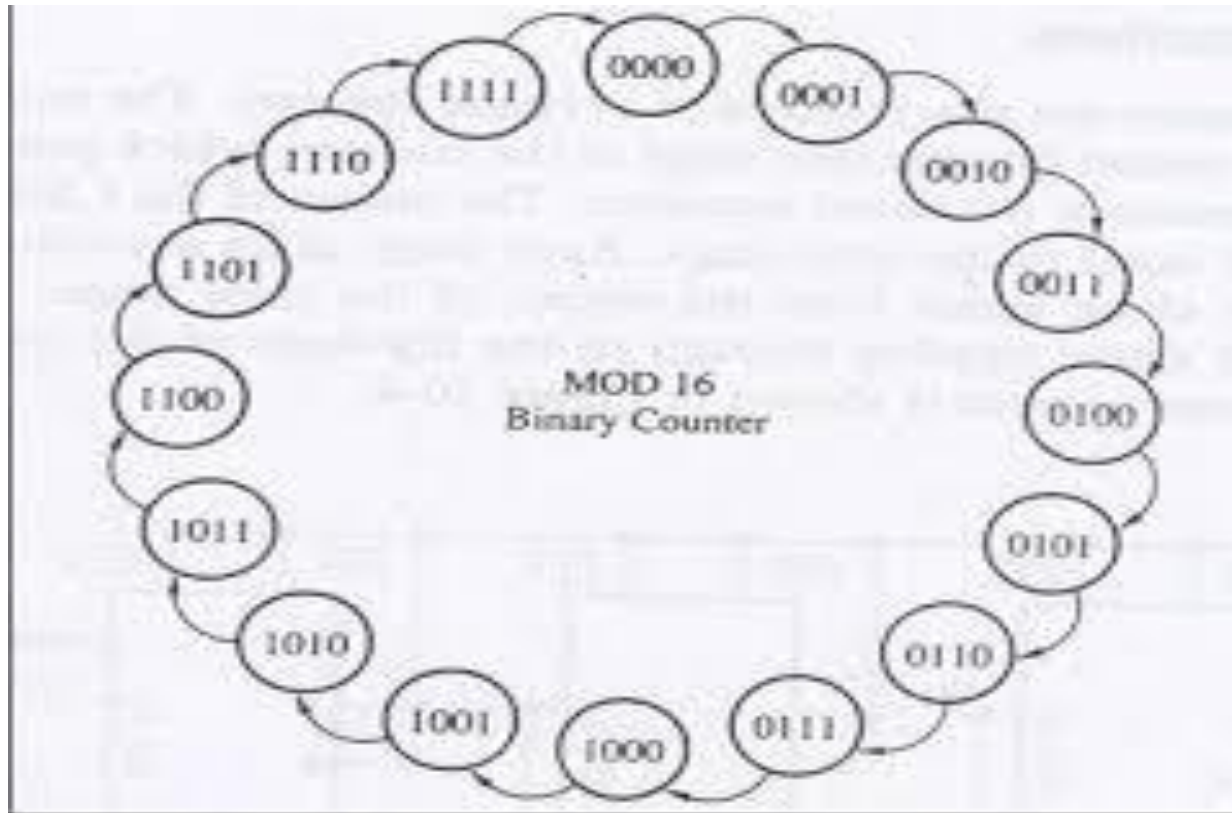5-11 Frequency Division and Counting


- State Transition diagram of MOD 16 Up Counter



- Internal Circuit of MOD 8 Down Counter

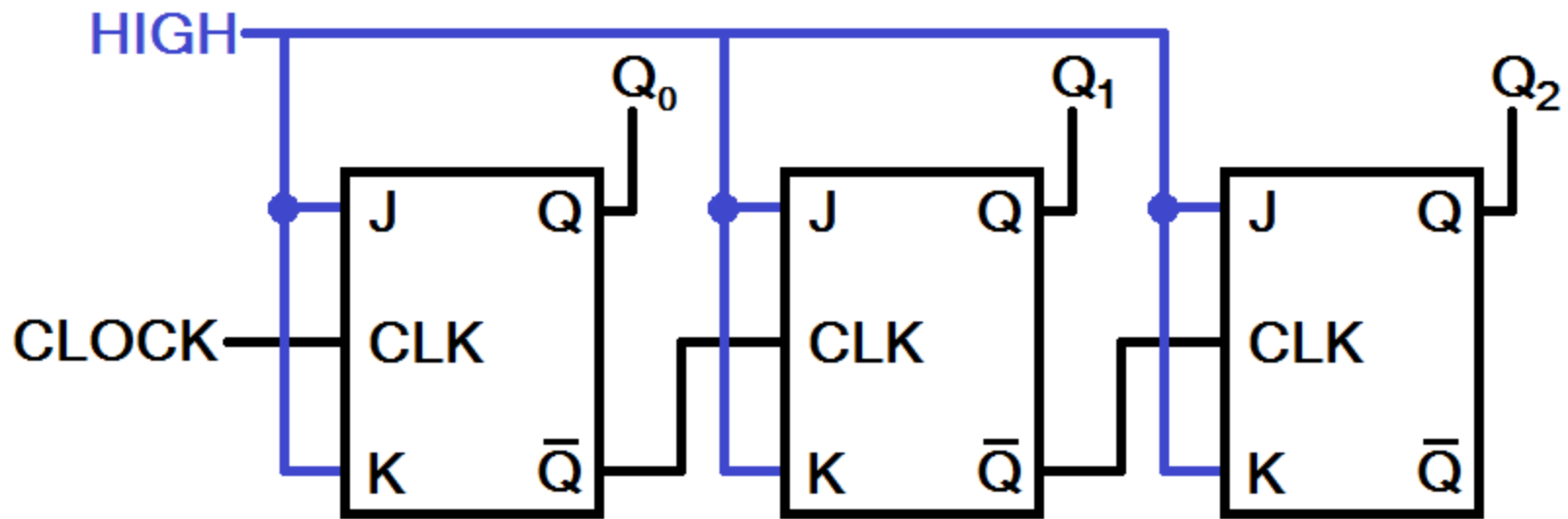

 
- Outputs will count from 111 to 000 or 7 to 0.



Timing Diagram of a 3bit Down Counter

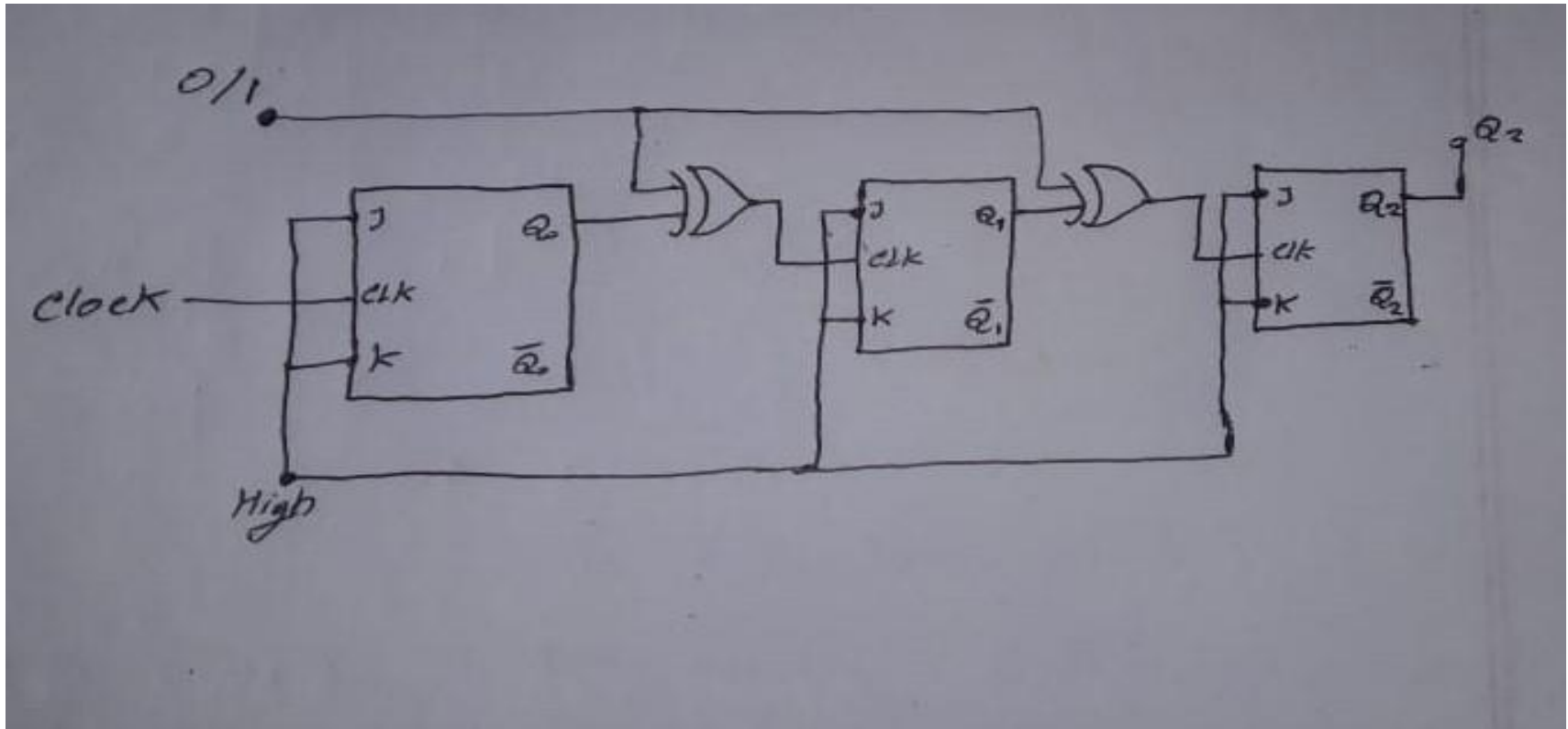5-11 Frequency Division and Counting

- Internal Circuit of MOD 8 Up/Down Counter



- If $S=0$ then clock of 2nd FF is Q_0 and clock of 3rd FF is Q_1 , So it is Mod 8 Up counter.
- If $S=1$ then clock of 2nd FF is \bar{Q}_0 and clock of 3rd FF is \bar{Q}_1 , So it is Mod 8 Down counter.

Question 1

Consider a counter circuit that contains six FFs wired in the arrangement Q5Q4Q3Q2Q1Q0

- (a) Determine the counter's MOD number.
- (b) Determine the output frequency in KHz when the input clock frequency is 1 MHz.
- (c) What is the range of counting states for this counter?
- (d) Assume a starting state (count) of 001001. What will be the counter's state after 129 pulses?

Question 2

A 20-kHz clock signal is applied to a J-K flip-flop with $J=K=1$. What is the frequency of the FF output waveform?

Question 3

- a) How many FFs are required for a counter that will count 0 to 255?
- b) What is the MOD number of the counter?

Question 4

- a) What is the frequency of the output of the eighth FF when the input clock frequency is 512 kHz?
- b) If this counter starts at 00011001, what will be its state after 520 pulses?

Question 5

A binary counter is being pulsed by a 256-kHz clock signal. The output frequency is 2 kHz.

- (a) Determine the MOD number.
- (b) Determine the counting range.

Question 6

- (a) How many FFs are required to build a binary counter that counts from 0 to 1023?
- (b) Determine the output frequency in Hz of this counter for an input clock frequency of 2 MHz.
- (c) What is the counter's MOD number?
- (d) If the counter is initially at zero, what count will it hold after 2060 pulses?

Question 7

Consider a MOD 16 up counter for the following questions:

- If the counter is initially at 1011 state, determine the output state after 83 pulses.
- If the input frequency of the clock signal is 10 MHz, what is the output frequency in KHz.
- Draw the state transition diagram of the counter.

Question 8

A photo detector circuit is being used to generate a pulse each time a customer walks into a certain establishment. The pulses are fed to an eight-bit counter. The counter is used to count these pulses as a means for determining how many customers have entered the store. After closing the store, the proprietor checks the counter and finds that it shows a count of 00001001=9. He knows that this is incorrect because there were many more than nine people in his store. Assuming that the counter circuit is working properly.

- a) What could be the reason for the discrepancy?
- b) How can you overcome from the discrepancy?

5-12 Model Question about this chapter

Question 9: Draw the internal circuit of clocked JK flip-flop. Briefly describe the operation of the flip-flop.

Question 10: Draw the internal circuit of clocked D flip-flop. Briefly describe the operation of the flip-flop.

Question 11: Convert JK to D flip-flop. Briefly explain.

Question 12: Define Mod number of counter.

Question 13: What are PGT and NGT?

Question 14: What are up and down counter?

5-12 Model Question about this chapter

Question 15: Draw the internal circuit of clocked S-C flip-flop. Briefly describe the operation of the flip-flop.

Question 16: Draw the internal circuit of NAND Latch. Briefly describe the operation of the Latch.

Question 17: Draw the internal circuit of NOR Latch. Briefly describe the operation of the Latch.

Question 18: Draw the internal circuit of MOD 8 up counter using J-K flip-flops. Briefly describe the operation of the counter.

5-12 Model Question about this chapter

- **Question 19:** Draw the internal circuit of MOD 16 up counter using J-K flip-flops. Briefly describe the operation of the counter.
- **Question 20:** Draw the internal circuit of MOD 8 down counter using J-K flip-flops. Briefly describe the operation of the counter.
- **Question 21:** Draw the internal circuit of MOD 16 down counter using J-K flip-flops. Briefly describe the operation of the counter.
- **Question 22:** Draw the internal circuit of MOD 8 up/down counter using J-K flip-flops & logic gates. Briefly describe the operation of the counter.