



UNIVERSITY OF ASIA PACIFIC

Department of Computer Science & Engineering

Course Title : Digital Logic & System Design Lab

Course Code : CSE 210

Experiment No. : 05

Experiment Name : **Implement and verify SR Latch with NAND and NOR gate.**

Date of Performance : 15-02-2022

Date of Submission : 17-02-2022

Submitted by:

Name : Sheikh Nafez Sadnan

Reg. No. : 20101106

Roll No. : 106

Section : B₍₂₎

Submitted To:

Shammi Akhtar

Assistant Professor

Department of CSE

University of Asia Pacific

A.

Problem Statement: Implement and verify SR Latch with NAND and NOR gate.

Instruments (Used in This Experiment):

- i. IC-7400 (NAND GATE)
- ii. IC-7402 (NOR GATE)
- iii. Wires
- iv. Trainer board

Truth Table:

SR Latch with NAND gate:

Input		Output	State
S	R		
0	0	$Q=Q'=1$	Invalid
0	1	1	Set
1	0	0	Reset
1	1	Q_0	No Change

SR Latch with NOR gate:

Input		Output	State
S	R		
0	0	Q_0	No Change
0	1	0	Reset
1	0	1	Set
1	1	$Q=Q'=0$	Invalid

Logic Diagram:

NAND Gate:




NOR Gate:




Circuit diagram of SR Latch with NAND gate:

When $S=0$, $R=1$ (SET)

 


When $S=1$, $R=0$ (RESET)

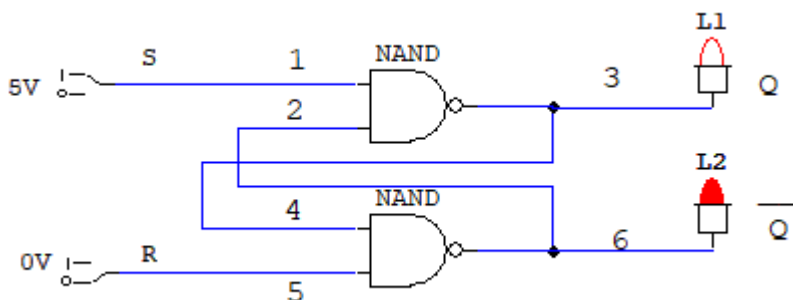


Circuit diagram of SR Latch with NOR gate:

When $S=0$, $R=1$ (RESET)

 

When $S=1$, $R=0$ (SET)

 

Discussion: In this experiment, we implemented and verified SR Latch with NAND and NOR gate. Security protocols were strictly maintained during the experiment. We verified our circuits by uses of truth table.